

# **VHDL Based Simulation of a Sigma-Delta A/D Converter**

**Martin Schubert**

FH Regensburg, FB Elektrotechnik, Seybothstr. 2,

D-93053 Regensburg, Germany

Email: [martin.schubert@e-technik.fh-regensburg.de](mailto:martin.schubert@e-technik.fh-regensburg.de)

# About the MixED Method

- MixED = Mixed-signal Event Driven
- Network of controlled sources
- Source voltages and output impedances are user-definable functions
- Implicit backward Euler integration of DEQ for capacitive and inductive loads
- Output of a controlled source is triggered not before input data is stable

# Academic Aspects

- Individual time stepping of each node
- Single kernel solver
- Iterations occur for nonlinear devices (e.g. CMOS inverter) and networks with more than 1 analog nodes between sources
- Convergence behavior for such networks of individually acting sources is subject to research

# Practical Aspects

- A/D and D/A converters
- PLL's (spec. if they have digital ports only)
- Fits in standard environments (DRC, Synthesizer)
- Models can be given as „black boxes“ to customers that have digital VHDL only
- No need to buy nor learn VHDL-AMS

# Problems / Features


- Numerical stability depends on models
- Moderate nonlinearities only (e.g. CMOS digital gates)
- Range of applications:  
academically probably <1% of VHDL-AMS  
practically many relevant mixed-signal  
circuits:  $\Sigma\Delta$ -modul., PLL, CMOS gates,  
OpAmp, SC, ...

# **Goal here: Verification of the VHDL Based MixED Simulation Module**


- **By comparison to simulated data**
- **By comparision to experimental data**
 
# Suitable Applications

Mostly digital circuits with some simple analog functions, as offered e.g. by the Institute for Microelectronics Stuttgart (IMS) [8].




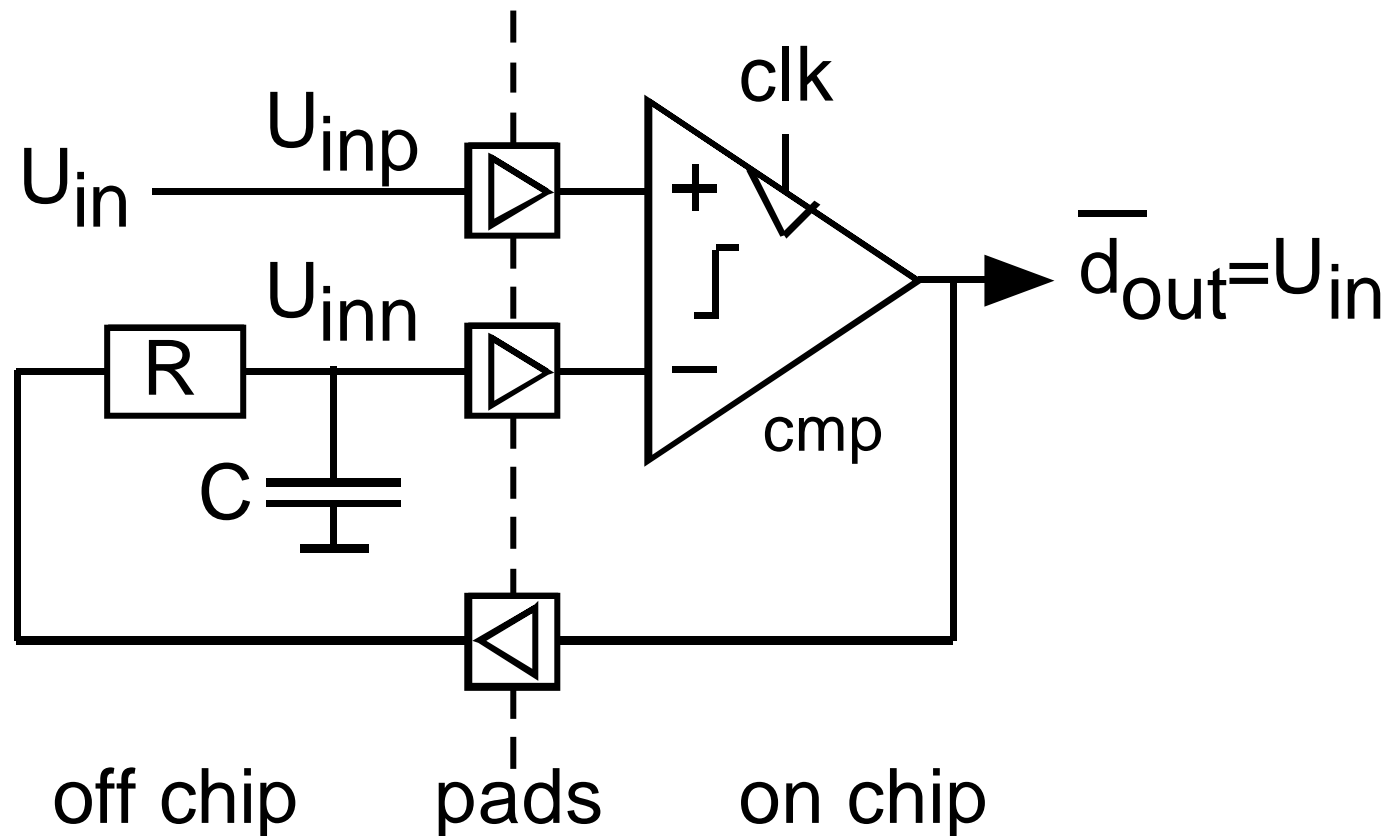
# Application: Sigma-Delta Modulator for A/D Conversion






# MixED vs. Pspice-AD Simulation

  


# Computing the average of the Pseudo-Random Bit Stream

- Average of  $d_{out}$ :  $\bar{d}_{out} = N / L$
- Corresp. Voltage:  $U_{out} = a \cdot \bar{d}_{out} + b$
- Filter:  $decimator\_out(n) = \sum_{i=0}^{L-1} d_{out}(n-i)$


# Measurement Setups

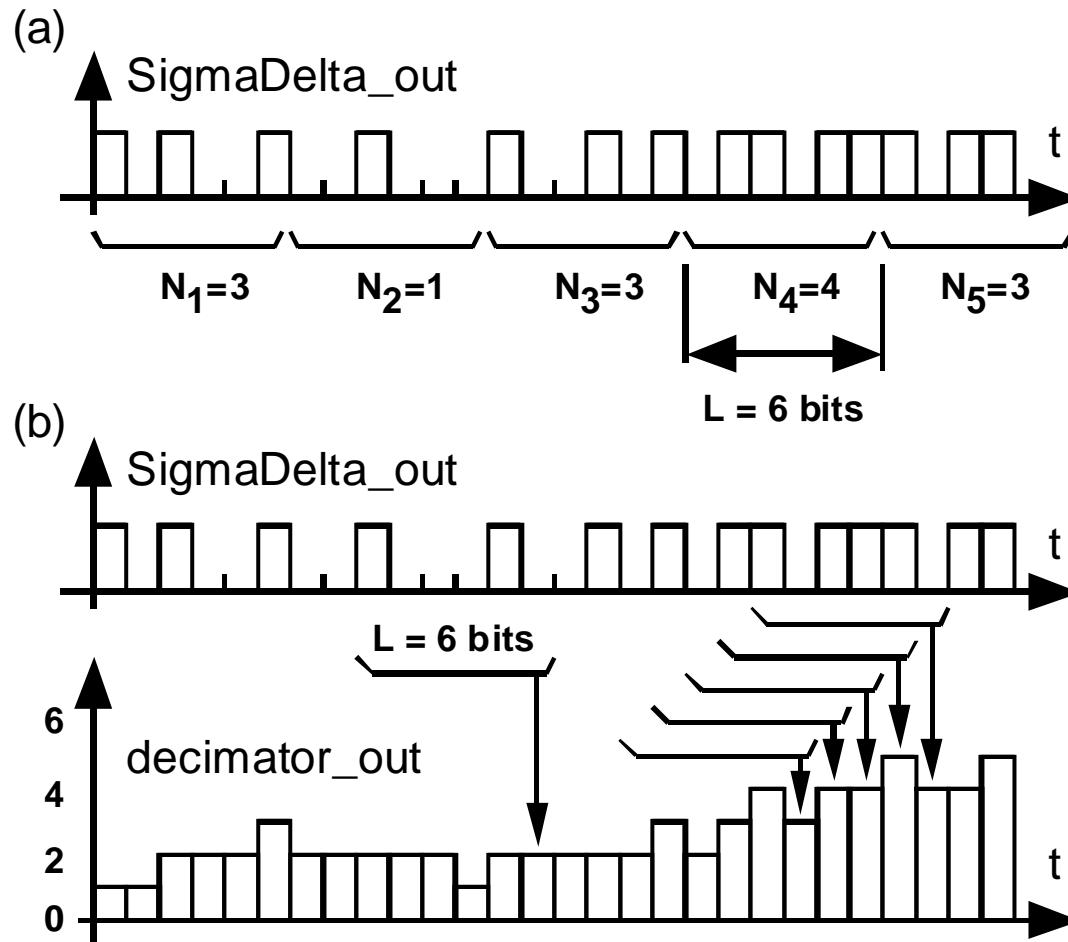

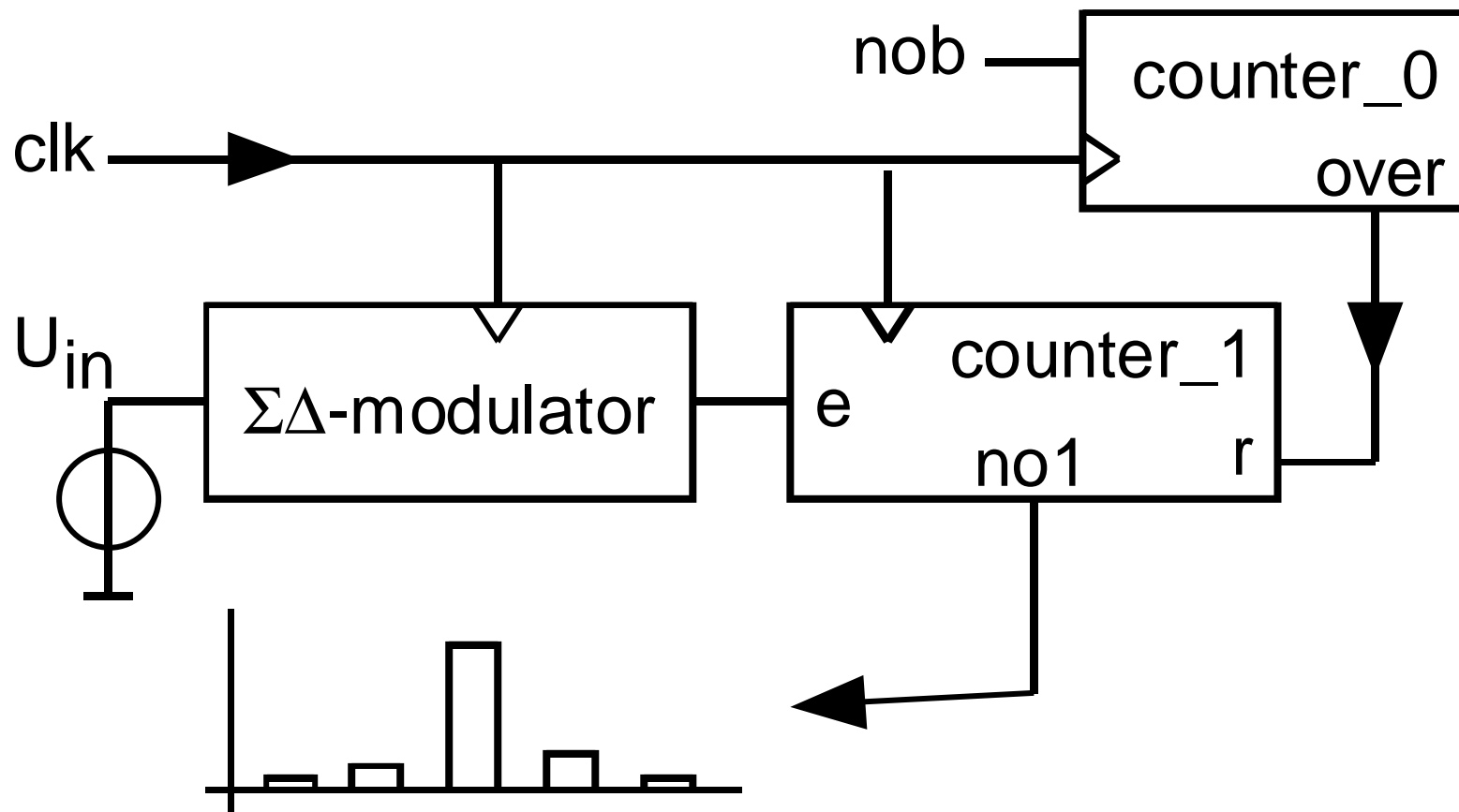
# Experimental Setup: Counters Used for Decimation



 
# Simulated Setup: Moving Averager Used for Decimation



# Experimental statistics

 

 
# Simulated $y_{out}/u_{in}$ Characteristics



Horizontal niveaus are due to the dead zone problem [11]


# Err: Output Voltage - Input Voltage

 

The maxima around  $U_{in}=2.5$  V illustrate the dead zone problem



 
# CPU Power Consumed with 8 Bit Averager at $f_{\text{clk}}=20\text{KHz}$




733MHz Intel Pentium III Processor und Windows NT 4.0
 
# CPU Power Consumed at with $2^{15} = 32768$ Bit Averager at $f_{clk}=20\text{KHz}$




733MHz Intel Pentium III Processor und Windows NT 4.0

# New Device: Clocked Comparator

 

(a) Asynchronous Comparator, (b) Clocked Comparator
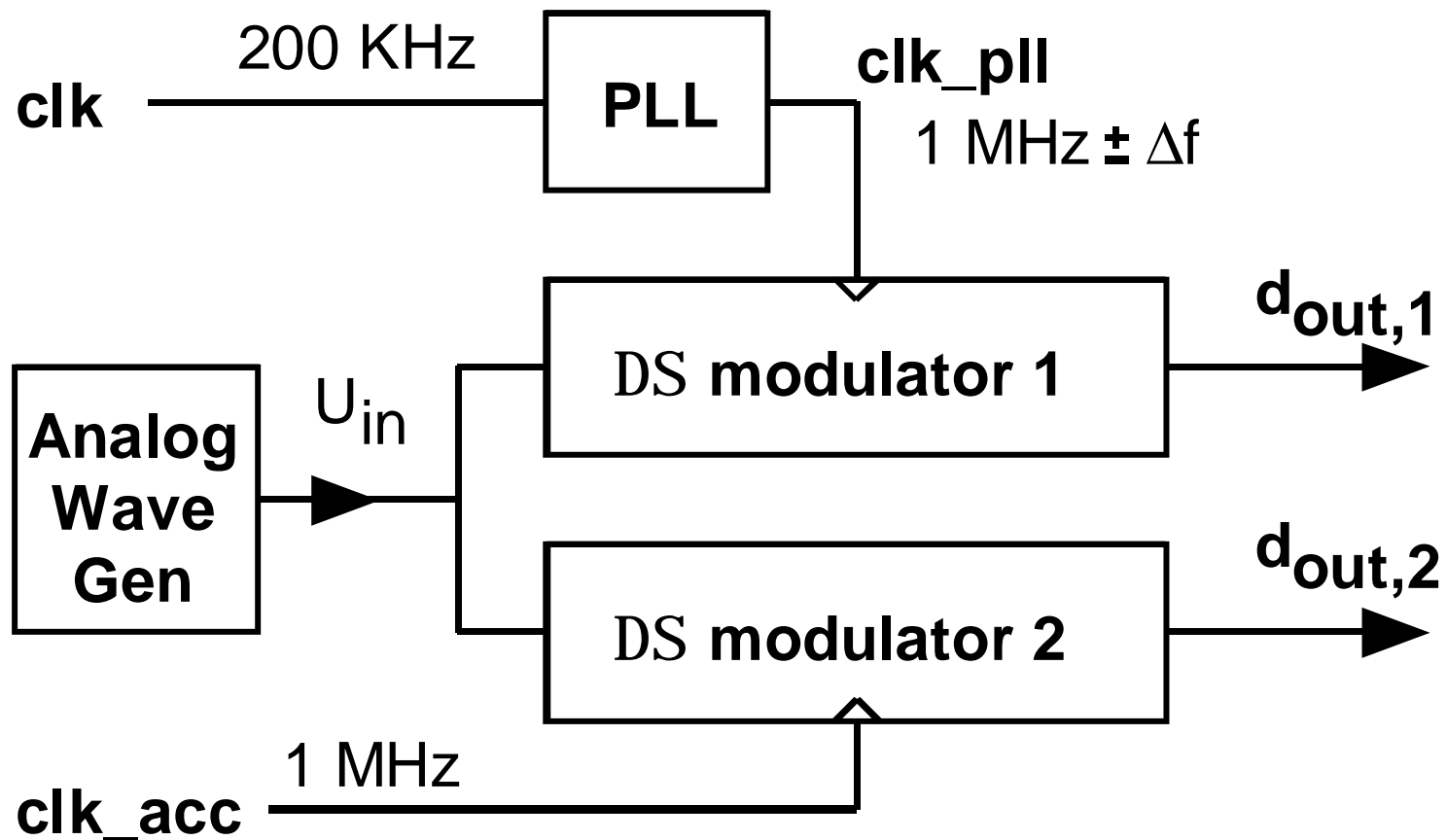
# Progress: System Composed of PLL and $\Sigma\Delta$ Already Simulated



# Employed Phase-Locked Loop [7]

