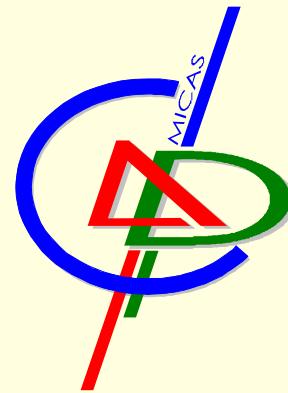


# Modeling and Simulation of a $\Sigma$ - $\Delta$ DAC using VHLD-AMS



Martin Vogels, Bart De Smedt, Georges Gielen  
ESAT - MICAS, K.U.Leuven



# Introduction

---

- ADC
  - $\Sigma - \Delta$  ADC very popular for mid-range performance (typ. 16 bit, 2 MHz)
  - flash, SAR for high-frequency or high-accuracy
- DAC
  - flash most common
  - $\Sigma - \Delta$  DAC has advantage of low area



# Overview


---

- DAC structure
  - noise shaper
  - thermo decoder
  - current cell array
- Nonidealities
- Evaluation Environment
- Illustration
- Conclusion



# Structure of a $\Sigma - \Delta$ DAC


---

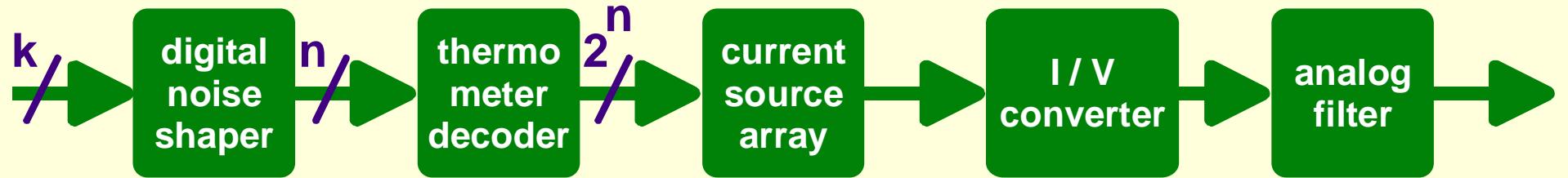

- Truncation ( $k > n$ ) :  
⇒ relatively small area for current source array
- $\Sigma - \Delta$  loop shapes quantization noise



# The digital noise shaper

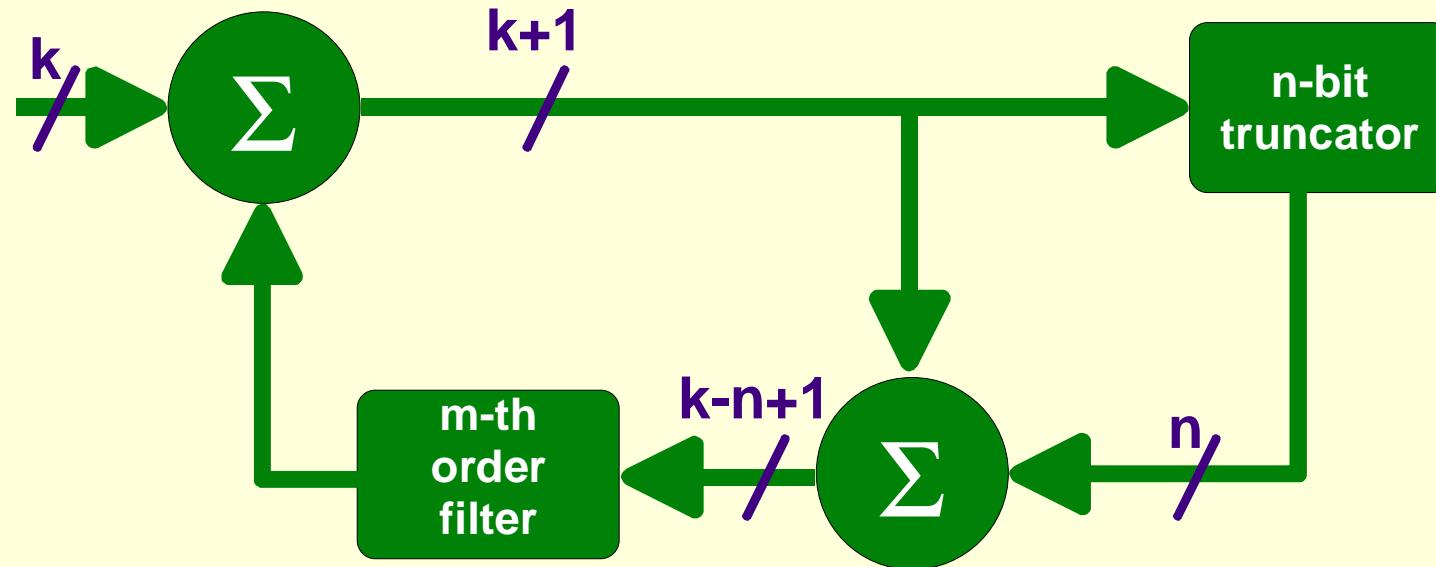

$$Y(z) = X(z) + (1 - z^{-1})^m E(z)$$

- Limiter prevents overload in filter
- Digital word vs. integer
- Delay in feed-back loop (asynchronous digital logic)



# The thermometer decoder

Fast conversion  
from analog to  
digital

$y[0] : 5$

standard	barrel shift	data weighted averaging
1 2 3 4	1 2 3 4	1 2 3 4
5 6 7 8	5 6 7 8	5 6 7 8
9 10 11 12	9 10 11 12	9 10 11 12
13 14 15 16	13 14 15 16	13 14 15 16

Performance  
limited by  
mismatch

$y[1] : 8$

1 2 3 4	1 2 3 4	1 2 3 4
5 6 7 8	5 6 7 8	5 6 7 8
9 10 11 12	9 10 11 12	9 10 11 12
13 14 15 16	13 14 15 16	13 14 15 16

Switching scheme  
important


$y[2] : 11$

1 2 3 4	1 2 3 4	1 2 3 4
5 6 7 8	5 6 7 8	5 6 7 8
9 10 11 12	9 10 11 12	9 10 11 12
13 14 15 16	13 14 15 16	13 14 15 16



# The current cell array

---

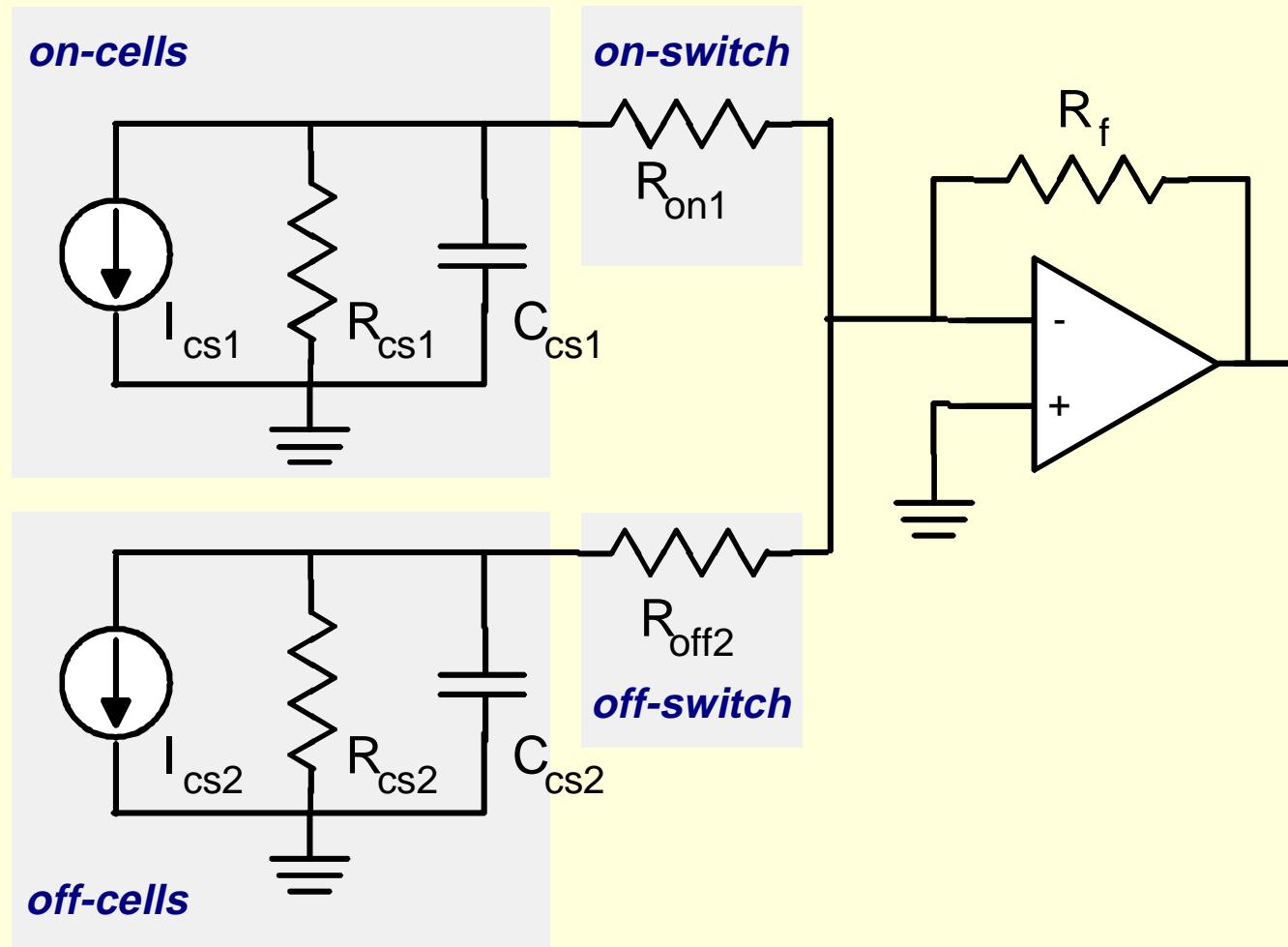


# The current cell array (cntd.)

---

	Lumped model	Distributed model
Evaluation time	Fast	Slow
Accuracy	Moderate	Good
DEM evaluation		



# Opamp model

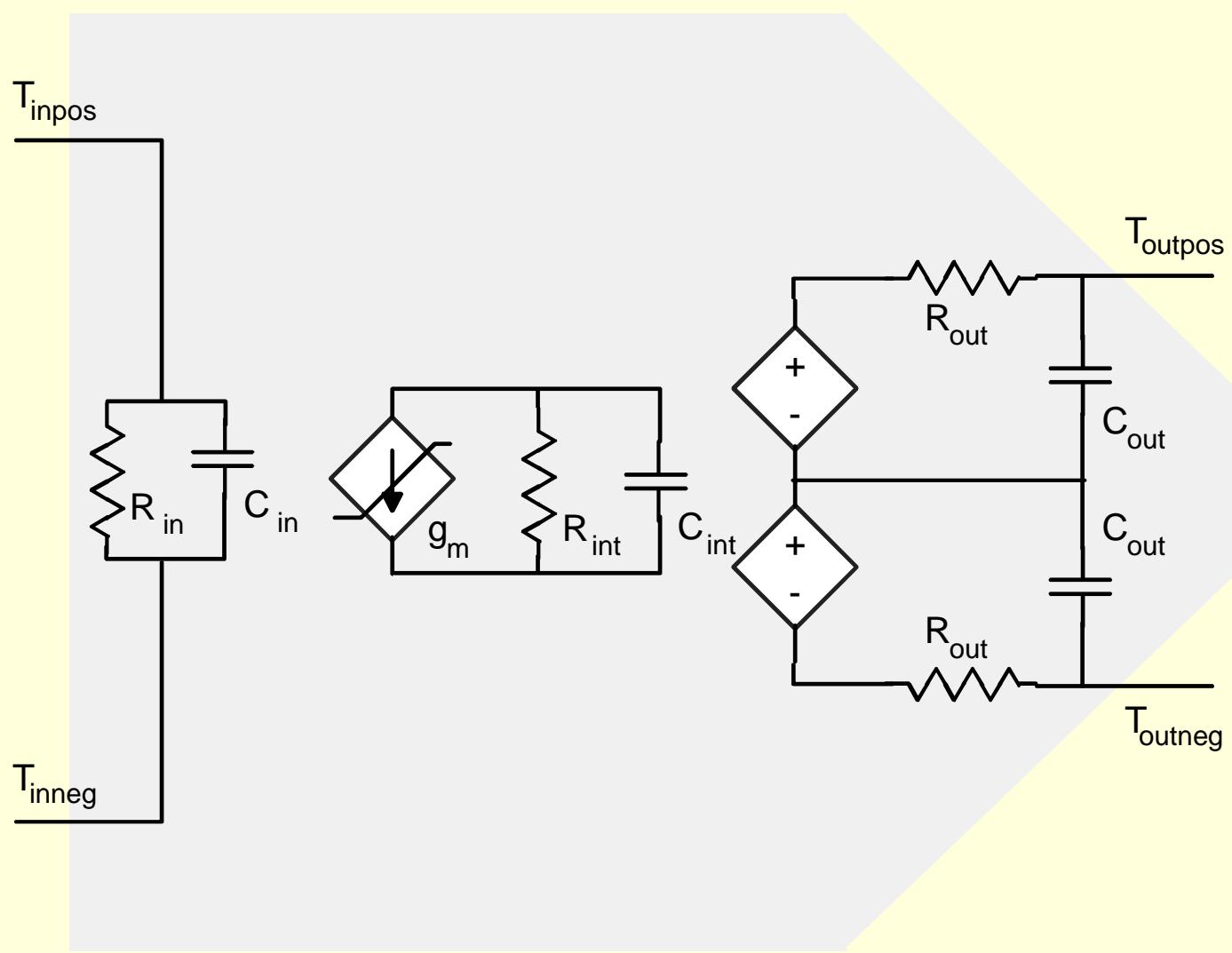

opamp specs

- $A_0$
- GBW
- SR
- first pole



# Overview

---

- DAC structure
- Nonidealities
  - current cell mismatch
  - settling
  - opamp slew rate
- Evaluation Environment
- Illustration
- Conclusion



# Current cell mismatch

- mismatch consists of systematic and random part

systematic mismatch	linear or quadratic gradient model
random mismatch	use random number generator



- use carefull layout techniques to reduce systematic mismatch
- random mismatch modeled using random number generators

$$\sigma\left(\frac{\Delta I_{out}}{I_{max-out}}\right) = \frac{1}{2\sqrt{NoLevels}} \cdot \sigma\left(\frac{\Delta I_{cell}}{I_{cell}}\right) \sqrt{K}$$



# Settling of the current cells

---

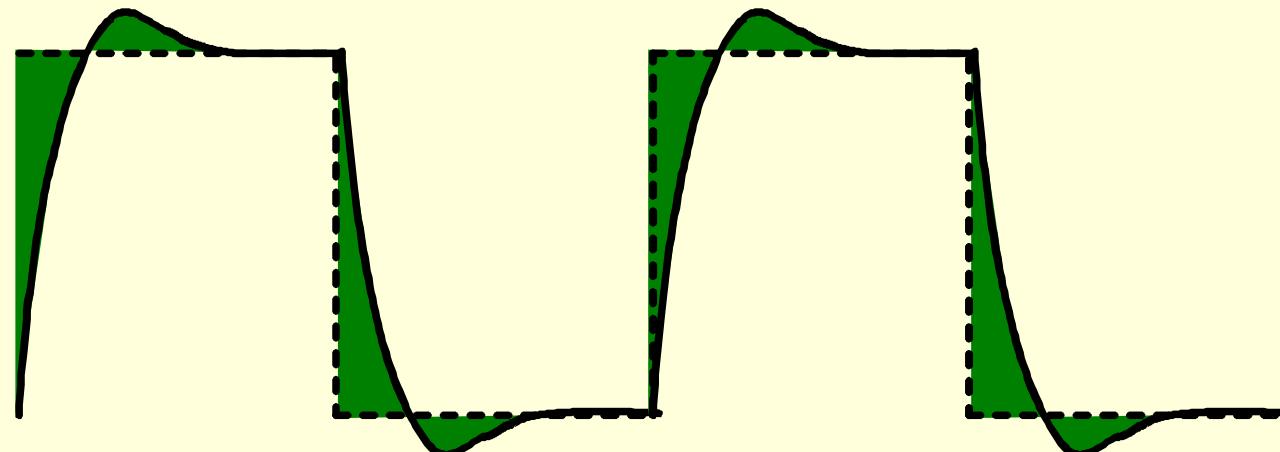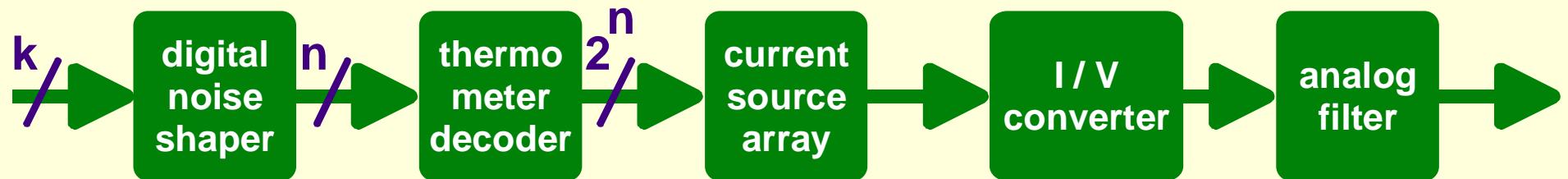

# Settling of the current cells

---

- linear analysis

- transfer from switching current cell to output voltage (simplified)

$$\frac{V_{out}}{I_{cell}} = H_b(s) = \frac{A_f}{s^2 + 2.s.\omega_n.\zeta + \omega_n^2}$$

- error due to settling :

$$e_{\max} = \frac{1}{2.\text{NoLevels}} \int_0^{\frac{1}{f_s}} \left( h_b(t).u(t) - \frac{1}{\text{NoLevels}} \right) dt$$

- this results in a noise power that equals :

$$e_{rms}^2 = \frac{1}{e_{\max}} \cdot \int_0^{e_{\max}} e^2 \cdot de = \frac{e_{\max}^2}{3}$$

- nonlinear analysis

- momentary values for different components depend on the input signal

⇒ transient analysis



# Opamp's slew rate

---

- opamp's slewing modeled by limiting the internal maximal current
- slew rate affects the settling behavior  
    ⇒    similar calculation method
- linear analysis results in ( $SR_n = SR_p$ ) :

$$e_{\max} = \frac{f_s}{2.\text{NoLevels}} \cdot \frac{1}{SR} \cdot \frac{1}{\text{NoLevels}}$$



# Overview

---

- DAC structure
- Nonidealities
- Evaluation Environment
- Illustration
- Conclusion




# Requirements for evaluation environment

---

- easy to plug-in specific models for different blocks
- automate simulation and post-processing
- flexibility towards the user to modify post-processing algorithms
- clearly log and track the ongoing evaluation process  
(also as documentation for later)



# Evaluation environment

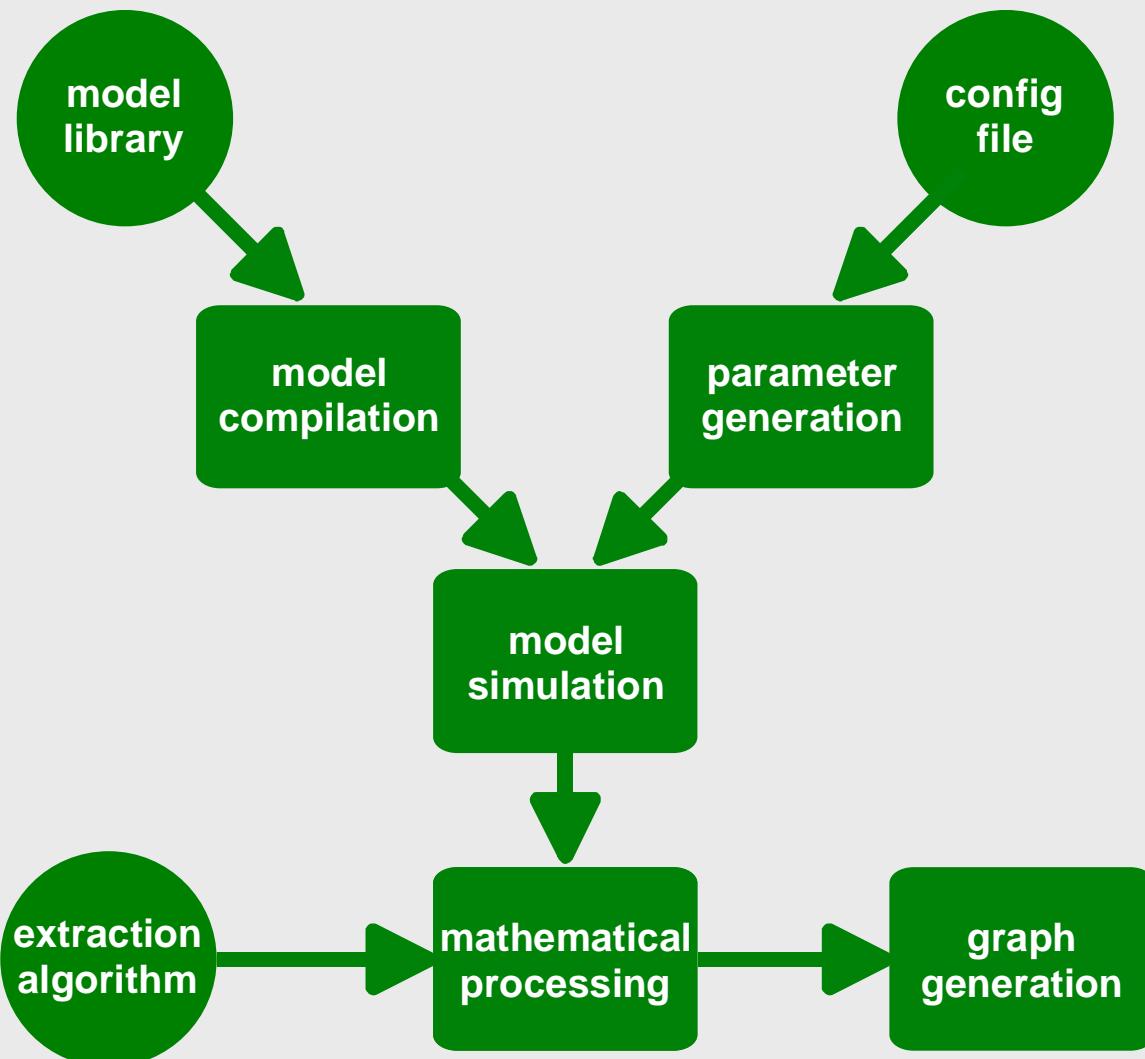

*glue : vamsSweep*



# Evaluation environment : example


## *config file*

```
% vamsSweep      v1.0.2  configuration file
entityName
architectureName
fixedVariableNames
fixedVariableValues
{samp, freq, rf }
{0.25e0, 1.0e3, 5.0e3}
sweepVariableNames
{pcin}
sweepType
log
sweepNoP
10
sweepStart
1.0e-12
sweepStop
1.0e-11
```

## *evaluation results*

1.000000e-12	5.3894127e+01
1.322376e-12	5.4098707e+01
1.748679e-12	5.4182483e+01
2.312411e-12	5.4822368e+01
3.057877e-12	5.5453887e+01
4.043663e-12	5.5488050e+01

## *intermediate result*

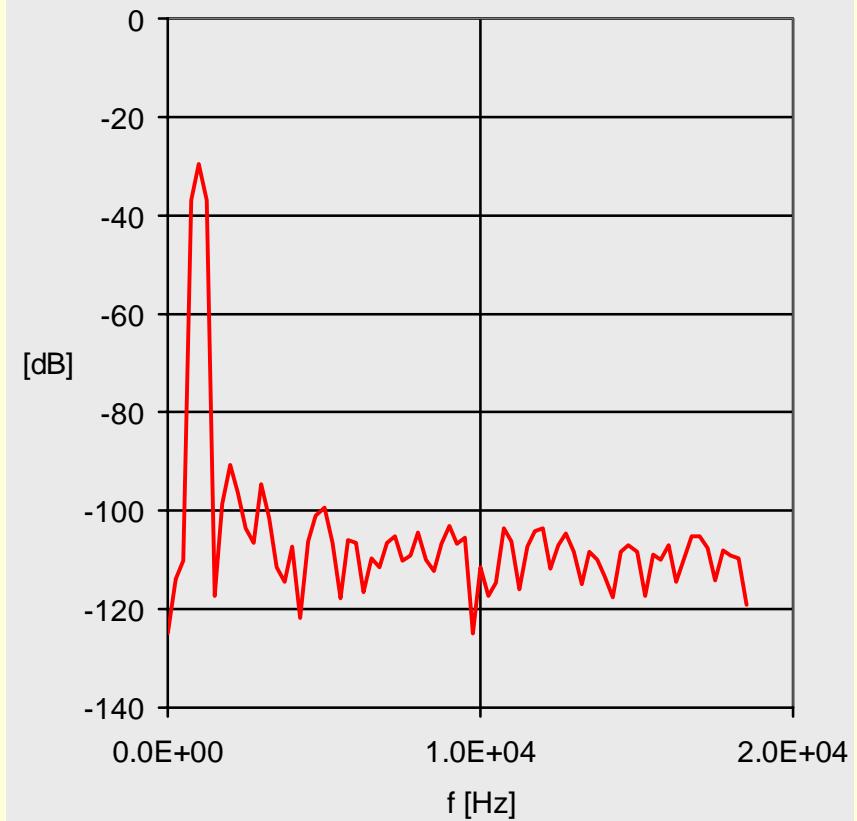


# Overview

---


- DAC structure
- Nonidealities
- Evaluation Environment
- Illustration
- Conclusion



# Slew Rate Simulated

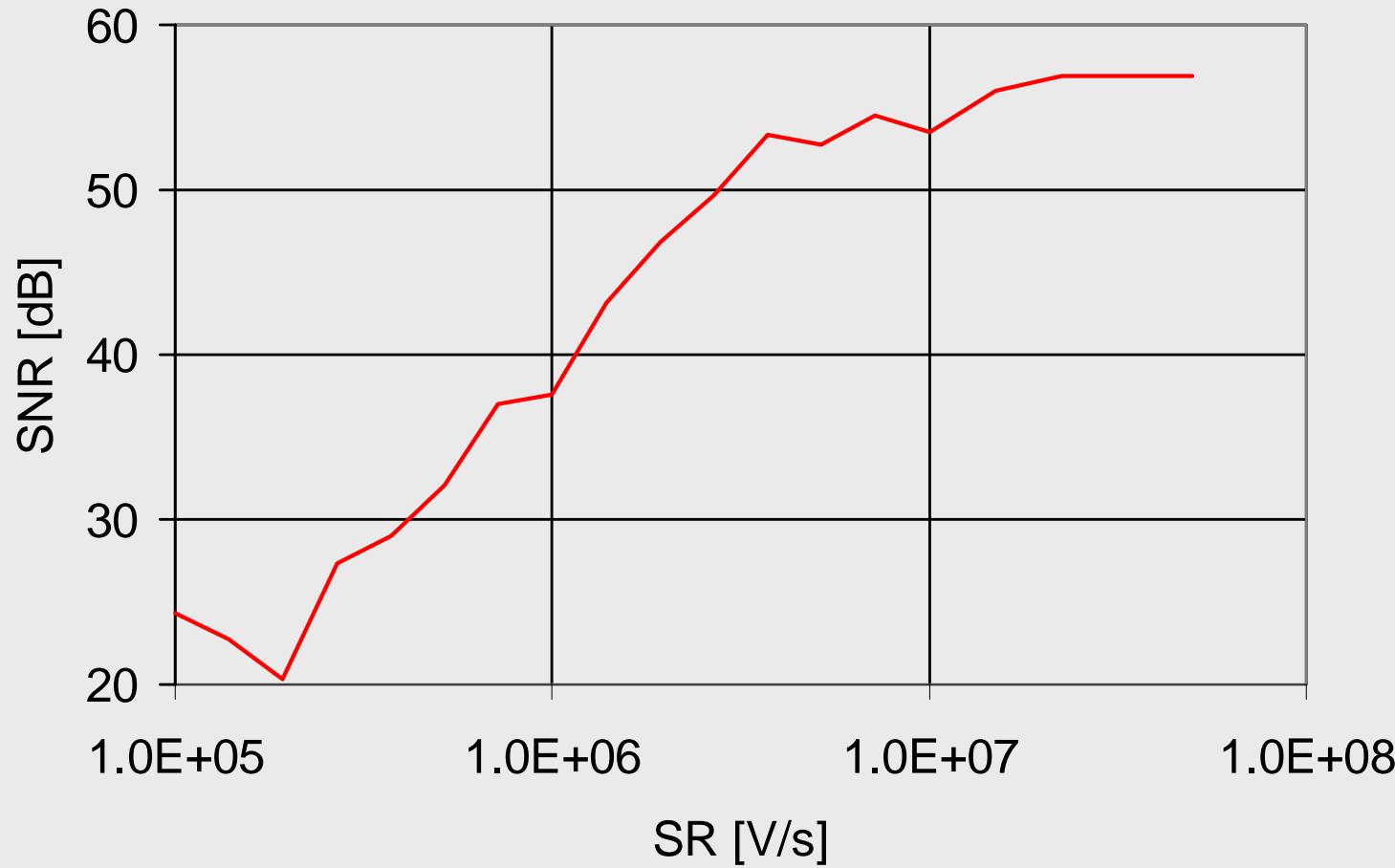


# Input Capacitance Variation Simulated

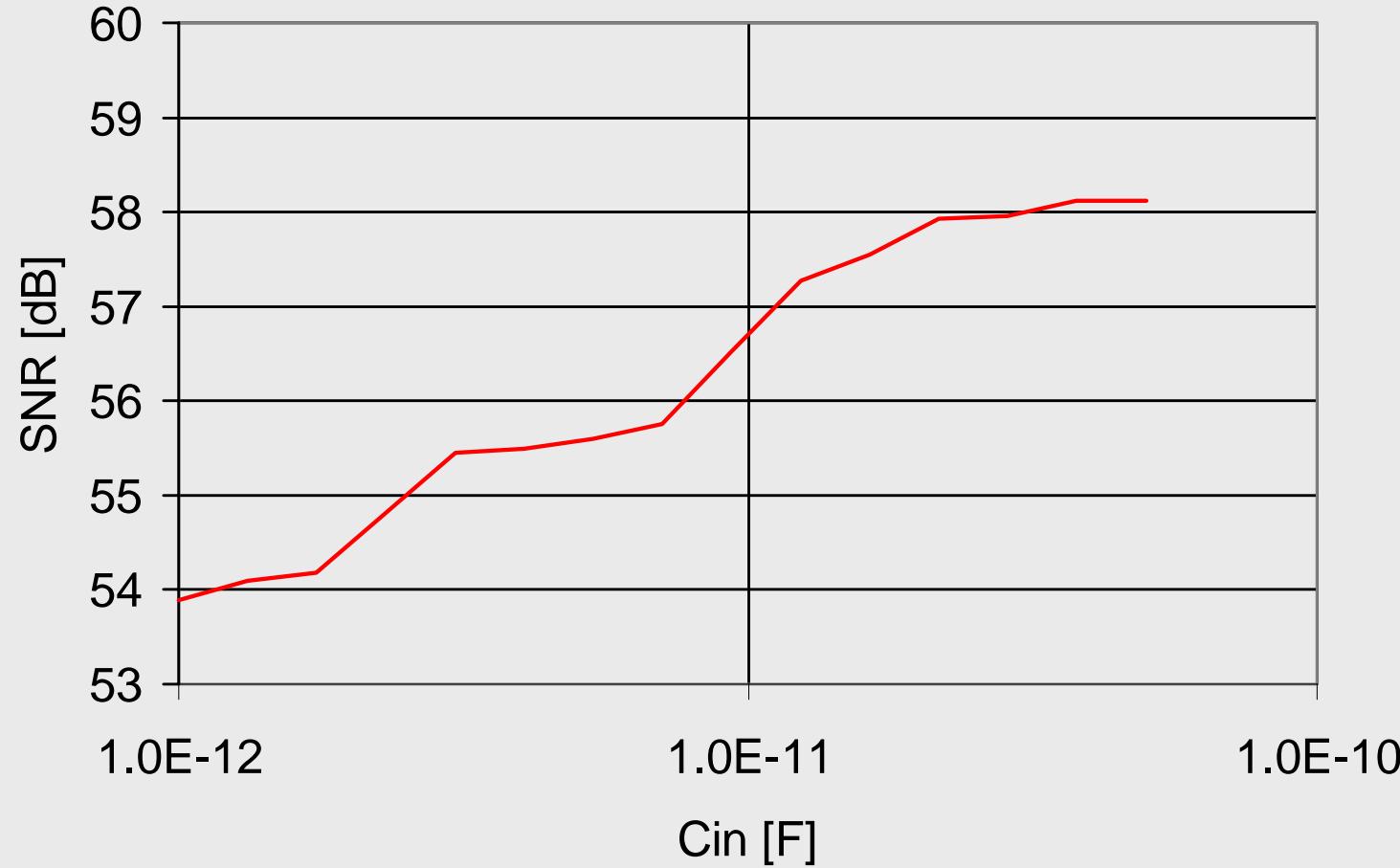

# Current Cell Mismatch Simulated

---

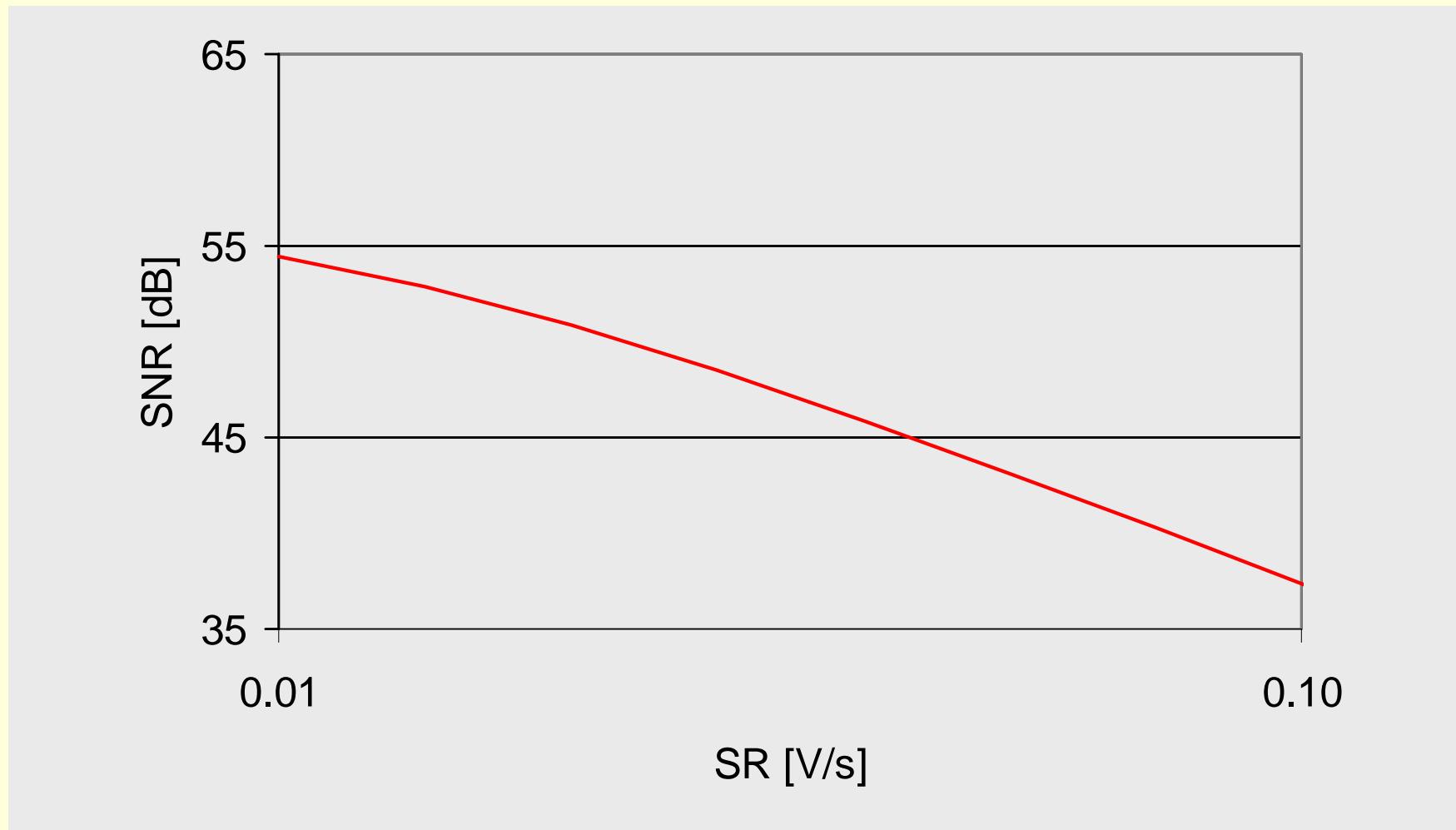

# Conclusions

---

- Generation of a library for  $\Sigma - \Delta$  DAC building blocks
- Identification and evaluation of the influence of the dominant DAC imperfections on SNR
- Setup of a flexible evaluation environment

